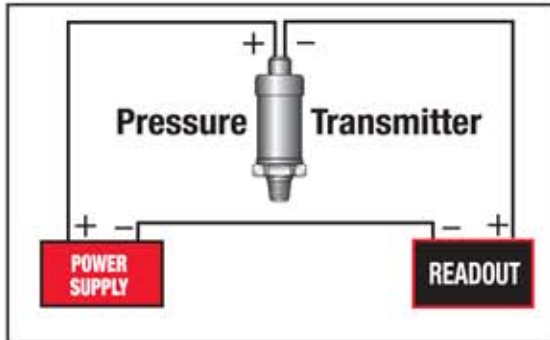
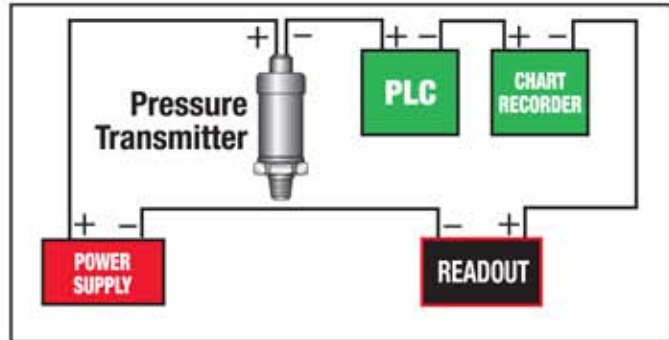


The Minimum Power Supply Voltage Required for a 2 Wire 4 mA to 20 mA Loop



Single instrument 2 wire current loop



Multiple instrument 2 wire current loop

For the single instrument 2 wire current loop, the minimum power supply voltage is equal to the required voltage across the transmitter plus the voltage drop across the instrumentation plus the voltage drop caused by the resistance of the wiring.

As an example, for a 100 series (4 mA to 20 mA output) pressure transmitter, $V_{transmitter} = 10 \text{ Vdc}$

$V_{wiring} = \text{Resistance of the wiring (handbook data)} \times 20 \text{ mA maximum current flow in the circuit}$. If the instrumentation has an input resistance of 250Ω and if the resistance of the wiring is minimal (100 ft of 24 AWG leadwire has less than 0.6Ω (negligible) of resistance), then the calculation including the leadwire is as follows:

$$V_{min} = 10 \text{ Vdc} + (250 \Omega) \times .020 \text{ Amp} + (0.6 \Omega) \times .020 \text{ Amp} = 15.012 \text{ Vdc}$$

The power supply must provide at least this voltage with the current consumption of $.020 \text{ Amp}$.

In a multiple instrument 2 wire current loop, if the second instrument also has an input resistance of 250Ω , then a second component on the right side of the equation must be included. In this case, the $V_{min} = 20.012 \text{ Vdc}$. A power supply of 24 Vdc , 1 Amp would be a typical choice.

If there is more than 1 transmitter loop operating off of the same power supply then the current ($.020 \text{ Amp}$) must be multiplied by the number of loops. It is recommended that the power supply provide 20 % to 30 % higher excitation voltage than that calculated above.

Load Limitations 4mA to 20mA output

$$V_{min} = 10V + (.020 \times R_L)$$

$$R_L = \text{Loop resistance } (\Omega)$$

$$R_L = R_S + R_W$$

$$R_S = \text{Sensor resistance } (\Omega)$$

$$R_W = \text{Wire Resistance } (\Omega)$$